PV101 Day 06 Student Print Packet

Troubleshooting and Hidden Fuses

Troubleshooting Worksheet

What is the system supposed to do?

_____

What is it doing now?

_____

What did your team check first?

_____

What voltage did you measure at the battery?

_____

Where did voltage stop?

_____

What evidence proved the fault?

_____

What did your team repair?

_____

Fault Isolation Table

Test Point	Expected	Measured	What It Means
PV module output			
Controller battery terminals			
Fuse input			
Fuse output			
Inverter input			
Load output			

Team Score Sheet

Criteria	Points	Score	Notes
Safe meter setup and PPE	10		
Logical power-flow tracing	20		
Accurate measurements recorded	20		
Correct fault identified	20		
Repair restored operation	15		
Team explanation	15		

Reflection

What slowed your team down?

_____

What assumption was wrong?

_____

What measurement gave you the answer?

_____

How will today's lesson change how you troubleshoot?

_____