Morning Quiz - Student Copy

PV101 Day 5 - Monday, July 13, 2026

Name: _____ Date: _____

Directions: Answer in plain language. Show calculations where needed. This is about verifying understanding, not being fancy.

1. In a solar/battery circuit, what does voltage describe?

Answer: _____

_____

2. What does current describe?

Answer: _____

_____

3. What is the formula for power in watts?

Answer: _____

_____

4. A 12.8 V battery is supplying 5 A to a load. About how many watts is that?

Answer: _____

_____

5. A 600 W inverter load on a 12 V battery can require roughly how much current before losses?

Answer: _____

_____

6. In a series connection, what usually adds: voltage or current capacity?

Answer: _____

_____

7. In a parallel connection, what usually stays the same and what increases?

Answer: _____

_____

8. What is a fuse actually protecting?

Answer: _____

_____

9. Where should the main load/inverter fuse be placed in a small battery system?

Answer: _____

_____

10. Why do we measure battery voltage before connecting equipment?

Answer: _____

_____

11. What is voltage drop?

Answer: _____

_____

12. Name one sign that a wire, crimp, or connection should be treated as unsafe.

Answer: _____

_____