PV102 Day 4 Morning Quiz

10 questions | 15 minutes | Independent work

PV102 | CTS Day 20 | Morning Quiz - Student
String design follows limits, temperature, and shade reality. | Thursday, August 6, 2026

Directions: Answer from your current knowledge. For written responses, use complete technical statements. If unsure, state the safe next action rather than guessing.

1. In series wiring, matching module voltage primarily:

- A. Adds
- B. Disappears
- C. Becomes AC
- D. Turns into resistance

2. In parallel wiring, matching branch current primarily:

- A. Adds
- B. Becomes zero
- C. Changes to frequency
- D. Removes voltage

3. The charge controller input limit is important because:

- A. Exceeding limits can damage equipment or create unsafe conditions
- B. It chooses wire color
- C. It makes sunlight brighter
- D. It stores energy

4. Shade on one module can affect:

- A. Only the paper worksheet
- B. Production and string behavior
- C. Lunch time only
- D. Nothing if the roof is new

5. Cold temperature generally makes PV voltage:

- A. Higher
- B. Always zero
- C. AC only
- D. Unrelated to design

6. Why should string design be checked before connecting equipment?

_____

_____

7. A controller allows 100 V max input. Should a design near 99 V be accepted without temperature check?

_____

_____

8. Name one reason parallel strings may require added protection.

_____

_____

9. What evidence from Day 2 matters most for shade design?

_____

_____

10. Write the Day 4 rule in your own words.

_____

_____