PV101 Day 8 Review Worksheet

Student copy | Use before the final

Day_08_PV101_Final_Review_and_Assessment_2026-07-16

Name: _____ Date: _____

Formula and units check

Write the power formula: _____

Calculate 24 W used for 3 h: _____ Wh

Convert 0.5 kW to watts: _____ W

In series, _____ adds. In parallel, _____ adds.

Verification chain

Put in order: evidence, symptom, conclusion, test.
Answer: _____

System path

Draw and label the basic PV-to-load energy path. Mark one fuse, one disconnect, and one meter point.

_____

_____

_____

Common misconceptions to correct

1. Wire color proves polarity. Correct / Incorrect: _____
Correction: _____

2. Continuity is tested on an energized circuit. Correct / Incorrect: _____
Correction: _____

3. Replacing a fuse proves the fault is repaired. Correct / Incorrect: _____
Correction: _____

4. Loads are the starting point for sizing. Correct / Incorrect: _____
Correction: _____

5. Cleanup is part of technical work. Correct / Incorrect: _____
Correction: _____